

# 浙江大学

\*\*\*\\*本科实验报告\\*\*\*\*

课程名称:	计算机组成
姓 名:	臧可
学 院:	计算机科学与技术学院
系:	计算机科学与技术系
专 业:	计算机科学与技术
学 号:	3180102095
指导教师:	姜晓红

2020年 05月 08日

## **\*浙江大学实验报告\***

课程名称: 计算机组成      实验类型: 综合

实验项目名称: Lab3-single cycle CPU implementation

学生姓名: 臧可      专业: 计算机科学与技术      学号: 3180102095

同组学生姓名: None      指导老师: 姜晓红

实验地点: 家里      实验日期: 2020年 05月 08日

# 一、实验目的和要求

---

Please do the project step by step according to the lab tutorial.

Object: Implement a combinational logic that enable the right switches on FPGA board control the eight Led lamp. Say, if switch being state on "010", then only the 2nd Led lamp is on.

Requirement: using the logical design way avoiding software coding like case statement.

## 1. Object: Design data path components and perform timing simulation

- ALU
- Register Files

### Requirement:

- ALU
  - Arrange the ALU of logic experiment eight
  - Logic diagram input and simulation
- Register Files
  - Optimization logic experiment Regs
  - Behavior description and simulation results

## 2. Object: Design a 18+ instruction data path

- Arithmetic logic component with general calculation function
- General purpose register
- Have the best possible path required for universal counting

### Requirement:

- Using logic schematic design to realize data path
  - ALU and Regs call modules designed by Exp04
- Replace Exp04's data path core
- This experiment is completed on the basis of Exp04

## 3. Object: Design a controller with 18+ instructions

- One of the main components of CPU
- Register transfer controller: code to command
- Design the controller test plan
- Design the controller test program

### Requirement:

- Design CPU controller
  - According to the analysis and discussion of the theory class, the controller designing the five data paths of the experiment
  - Schematic diagram or HDL description can be
    - But it must be described with a function expression structure
  - Simulation test controller module
- Integrate and replace the validated data path module
  - Replace the SCPU\_ctrl.ngc core in Experiment 5 (Exp05)

- Module name: Top\_OExp06\_OwnSCPU.sch
- Test controller module
  - Design test program (MIPS assembly) test:
- OP decoding test:
  - R-format, memory access instruction, branch instruction, branch instruction
- Operation control test: Function decoding test

#### 4. Object:Set top-level module


- New CPU with integrated replacement verification
- CPU logic symbols need to be modified

#### Requirement:

- implement no less than the following instructions
  - R-Type: add, sub, and, or, xor, nor, slt, srl \*, jr, jalr, eret;
  - I-Type: addi, andi, ori, xori, lui, lw, sw, beq, bne, slti
  - J-Type: J, Jal \*;
- Design test program (MIPS assembly) test CPU logic symbols

## 二、 实验内容和原理

### Logic schematic input design ALU

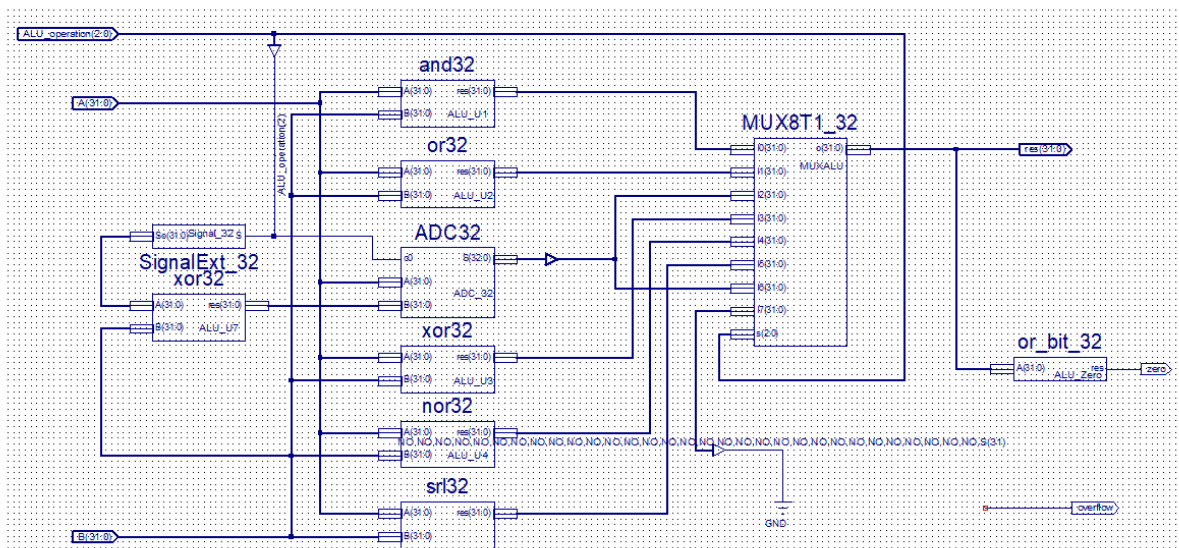

### Behavior description design Register files

```


1 module Regs(input clk,rst,L_S,
2               input [4:0] R_addr_A, R_addr_B, wt_addr,
3               input [31:0] wt_data,
4               output [31:0] rdata_A, rdata_B
5 );
6   reg [31:0] register[1:31];
7   integer i;
8
9
10  assign rdata_A = (R_addr_A == 0)?0:register[R_addr_A];
11  assign rdata_B = (R_addr_B == 0)?0:register[R_addr_B];
  
```

```

12
13
14     always@(posedge clk or posedge rst)
15         begin if(rst==1)
16             for(i=1;i<32;i=i+1)
17                 register[i] <= 0;
18             else if((Wt_addr != 0) && (L_S == 1)) //0地址保留给zero
19                 register[Wt_addr] <= wt_data;
20         end
21
22 endmodule

```
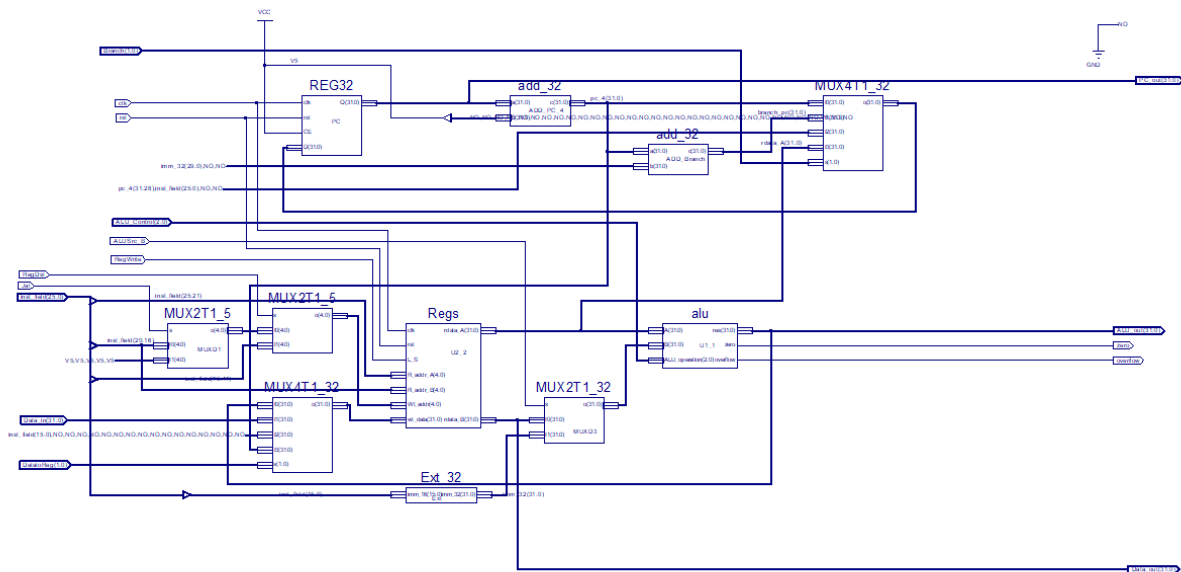
## Logic schematic input design Data\_path



## SCPU\_ctrl HDL description structure

```

1  module SCPU_ctrl_more(input [5:0] OPCODE,
2                          input [5:0] Fun,
3                          input MIO_ready,
4                          input zero,
5                          output reg RegDst,
6                          output reg ALUSrc_B,
7                          output reg [1:0] DatatoReg,
8                          output reg Jal,
9                          output reg [1:0] Branch,
10                         output reg RegWrite,
11                         output reg mem_w,
12                         output reg [2:0] ALU_Control,
13                         output reg CPU_MIO
14  );
15  `define
CPU_ctrl_signals{RegDst,ALUSrc_B,DatatoReg,Jal,Branch,RegWrite,mem_w,CPU_MIO,ALU_Control}
16      always@*begin
17          case(OPCODE)
18              6'b000000:begin

```

```

19         case(Fun)
20             6'b100000:begin `CPU_ctrl_signals =
13'b10000_00100_010;end //add
21             6'b100010:begin `CPU_ctrl_signals =
13'b10000_00100_110;end //sub
22             6'b100100:begin `CPU_ctrl_signals =
13'b10000_00100_000;end //and
23             6'b100101:begin `CPU_ctrl_signals =
13'b10000_00100_001;end //or
24             6'b000010:begin `CPU_ctrl_signals =
13'b10000_00100_101;end //srl
25             6'b101010:begin `CPU_ctrl_signals =
13'b10000_00100_111;end //slt
26             6'b100111:begin `CPU_ctrl_signals =
13'b10000_00100_100;end //nor
27             6'b100110:begin `CPU_ctrl_signals =
13'b10000_00100_011;end //xor
28             6'b001000:begin `CPU_ctrl_signals =
13'b10001_11000_000;end //jr
29             6'b001001:begin `CPU_ctrl_signals =
13'b10111_11100_010;end //jalr
30             default: begin `CPU_ctrl_signals =
13'b00000_00000_000;end
31         endcase
32     end
33     6'b100011:begin `CPU_ctrl_signals = 13'b01010_00100_010;end
//load
34     6'b101011:begin `CPU_ctrl_signals = 13'b01000_00010_010;end
//store
35     6'b000100:begin
36         if(zero==1'b1) `CPU_ctrl_signals = 13'b00000_01000_110;
37         else `CPU_ctrl_signals = 13'b00000_00000_110;
38     end //beq
39     6'b000101:begin
40         if(zero==1'b0) `CPU_ctrl_signals = 13'b00000_00000_110;
41         else `CPU_ctrl_signals = 13'b00000_01000_110;
42     end //bne
43     6'b000010:begin `CPU_ctrl_signals = 13'b00000_10000_000;end
//j
44     6'b000011:begin `CPU_ctrl_signals = 13'b00111_10100_010;end
//jal
45     6'b001111:begin `CPU_ctrl_signals = 13'b00100_00100_010;end
//lui
46     6'b001010:begin `CPU_ctrl_signals = 13'b01000_00100_111;end
//slti
47     6'b001110:begin `CPU_ctrl_signals = 13'b01000_00100_011;end
//xori
48     6'b001111:begin `CPU_ctrl_signals = 13'b01000_00100_001;end
//ori
49     6'b001100:begin `CPU_ctrl_signals = 13'b01000_00100_000;end
//andi
50     6'b001000:begin `CPU_ctrl_signals = 13'b01000_00100_010;end
//addi
51     6'b010000:begin `CPU_ctrl_signals = 13'b10000_11100_010;end
//eret
52     default: begin `CPU_ctrl_signals = 10'b00000_00000_000;end
53 endcase
54 end


```

```


55
56 endmodule

```

## SCPU

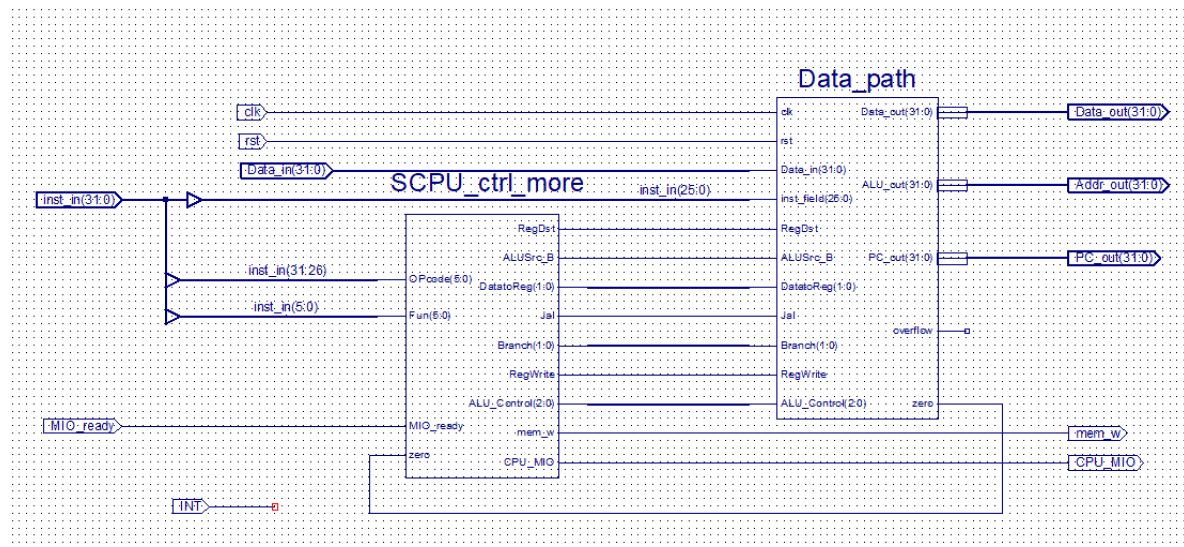

## Top

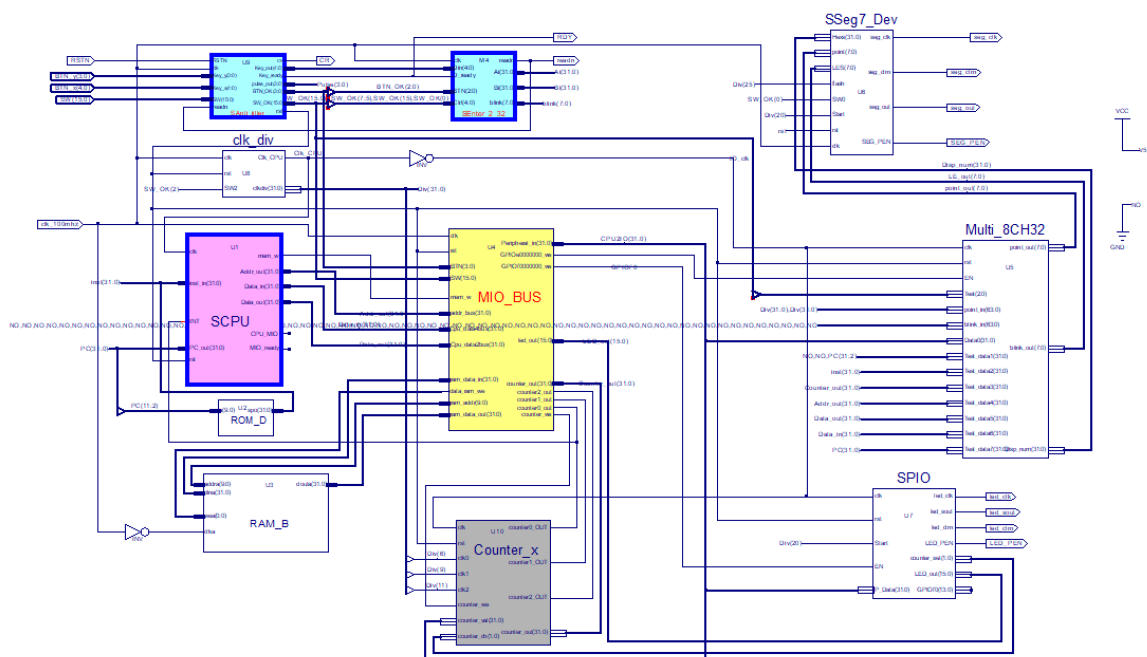

## 三、实验过程和数据记录及结果分析

### ALU

#### ALU Incentive code

```

1 initial begin
2     A = 0;
3     B = 0;


```

```

4      ALU_operation = 0;
5      #100;
6      A=32'hA5A5A5A5;
7      B=32'h5A5A5A5A;
8      ALU_operation =3'b111;
9      #100;
10     ALU_operation =3'b110;
11     #100;
12     ALU_operation =3'b101;
13     #100;
14     ALU_operation =3'b100;
15     #100;
16     ALU_operation =3'b011;
17     #100;
18     ALU_operation =3'b010;
19     #100;
20     ALU_operation =3'b001;
21     #100;
22     ALU_operation =3'b000;
23     #100;
24     A=32'h01234567;
25     B=32'h76543210;
26     ALU_operation =3'b111;
27
28     end

```

## ALU\_Simulation results

 

Simulation results are as expected

## Regs Files

### Regs Incentive code

```

1      initial begin
2          // Initialize Inputs
3          clk = 0;
4          rst = 0;
5          L_S = 0;
6          R_addr_A = 0;
7          R_addr_B = 0;
8          wt_addr = 0;
9          wt_data = 0;
10
11         // wait 100 ns for global reset to finish
12         #100;
13         rst = 1;
14         #40;
15         rst = 0;
16         L_S = 1;
17         wt_addr = 5;
18         wt_data = 32'hA5A5A5A5;


```

```

19         #20;
20         wt_addr = 6;
21         wt_data = 32'h55AA55AA;
22         #20;
23         wt_addr = 0;
24         wt_data = 32'hAAAA5555;
25         #20;
26         L_S = 0;
27         wt_data = 0;
28         R_addr_A = 5;
29         R_addr_B = 6;
30
31     end
32
33     always begin
34         clk=0;#10;
35         clk=1;#10;
36     end
37

```

## Regs simulation results

 

Simulation results are as expected

## Data\_path

### Data\_path Incentive code

```

1         initial begin
2             RegWrite = 0;
3             DatatoReg = 0;
4             Data_in = 0;
5             ALUSrc_B = 0;
6             ALU_Control = 0;
7             rst = 1;
8             Branch = 0;
9             clk = 0;
10            Jal = 0;
11            inst_field = 0;
12            RegDst = 0;
13
14            #40; rst=0;
15            #20;
16            //lw $5,11($6)
17            Jal = 0;
18            Branch = 0;
19            RegWrite = 1;
20            inst_field[25:21]=6; //rs
21            inst_field[20:16]=5; //rt

```



```
22     inst_field[15:0]=11;
23     RegDst = 0;
24     DatatoReg = 1;
25     Data_in = 32'haaaaffff;
26     ALUSrc_B = 1;
27     ALU_Control=2;
28     #20;
29     //lw $6,12($5)
30     inst_field[25:21]=5;
31     inst_field[20:16]=6;
32     inst_field[15:0]=12;
33     Data_in = 32'hffffaaa;
34     #20;
35     //sw $5,15($6)
36     RegWrite = 0;
37     inst_field[25:21]=6;
38     inst_field[20:16]=5;
39     inst_field[15:0]=15;
40     DatatoReg = 0;
41     Data_in = 0;
42     #20;
43     //add $7,$6,$5
44     RegWrite = 1;
45     inst_field[25:21]=6;
46     inst_field[20:16]=5;
47     inst_field[15:11]=7;
48     RegDst = 1;
49     ALUSrc_B = 0;
50     #20;
51     //sw $7,5($6)
52     RegWrite = 0;
53     inst_field[25:21]=6;
54     inst_field[20:16]=7;
55     inst_field[15:0]=5;
56     RegDst = 0;
57     ALUSrc_B = 1;
58     #20;
59     //sub $8,$5,$6
60     RegWrite = 1;
61     inst_field[25:21]=5;
62     inst_field[20:16]=6;
63     inst_field[15:11]=8;
64     RegDst = 1;
65     ALUSrc_B = 0;
66     ALU_Control=6;
67     #20;
68     //sw $8,0($6)
69     RegWrite = 0;
70     inst_field[25:21]=6;
71     inst_field[20:16]=8;
72     inst_field[15:0]=0;
73     RegDst = 0;
74     DatatoReg = 0;
75     ALUSrc_B = 1;
76     ALU_Control=2;
77     #20;
78     //and $8,$5,$6
79     RegWrite = 1;
```

```

80     inst_field[25:21]=5;
81     inst_field[20:16]=6;
82     inst_field[15:11]=8;
83     RegDst = 1;
84     ALUSrc_B = 0;
85     ALU_Control=0;
86     #20;
87     //sw $8,0($6)
88     RegWrite = 0;
89     inst_field[25:21]=6;
90     inst_field[20:16]=8;
91     inst_field[15:0]=0;
92     RegDst = 0;
93     ALUSrc_B = 1;
94     ALU_Control=2;
95     #20;
96     //or $8,$5,$6
97     RegWrite = 1;
98     inst_field[25:21]=5;
99     inst_field[20:16]=6;
100    inst_field[15:11]=8;
101    RegDst = 1;
102    ALUSrc_B = 0;
103    ALU_Control=1;
104    #20;
105    //sw $8,0($6)
106    RegWrite = 0;
107    inst_field[25:21]=6;
108    inst_field[20:16]=8;
109    inst_field[15:0]=0;
110    RegDst = 0;
111    ALUSrc_B = 1;
112    ALU_Control=2;
113    #20;
114    //slt $25,$9,$1
115    Branch = 1;
116    RegWrite = 0;
117    inst_field[25:21]=9;
118    inst_field[20:16]=1;
119    inst_field[15:0]=25;
120    RegDst = 1;
121    ALUSrc_B = 0;
122    ALU_Control=7;
123    #20;
124    //beq $6,$8,0
125    Branch = 0;
126    RegWrite = 0;
127    inst_field[25:21]=6;
128    inst_field[20:16]=8;
129    inst_field[15:0]=0;
130    RegDst = 0;
131    ALUSrc_B = 1;
132    ALU_Control=2;
133    #20;
134    //nor $8,$5,$6
135    RegWrite = 1;
136    inst_field[25:21]=5;
137    inst_field[20:16]=6;

```

```

138         inst_field[15:11]=8;
139         RegDst = 1;
140         ALUSrc_B = 0;
141         ALU_Control=4;
142         #20;
143     end
144
145     always begin
146         clk = 0; #20;
147         clk = 1; #20;
148         end

```

## Data\_path simulation results



Simulation results are as expected

## SCPU\_ctrl

### SCPU\_ctrl Incentive code

```

1     initial begin
2         // Initialize Inputs
3         OPCODE = 0;
4         Fun = 0;
5         MIO_ready = 0;
6         zero = 0;
7
8         // wait 20 ns for global reset to finish
9         #20;
10
11        // Add stimulus here
12        Fun = 6'b100000; //add



```


```

13      #20; Fun = 6'b100010; //sub
14      #20; Fun = 6'b100100; //and
15      #20; Fun = 6'b100101; //or
16      #20; Fun = 6'b000010; //sr1
17      #20; Fun = 6'b101010; //slt
18      #20; Fun = 6'b100111; //nor
19      #20; Fun = 6'b100110; //xor
20      #20; Fun = 6'b001000; //jr
21      #20; Fun = 6'b001001; //jalr
22      #20; OPCODE = 6'b000010; //j
23      #20; OPCODE = 6'b000011; //jal
24      #20; OPCODE = 6'b001111; //lui
25      #20; OPCODE = 6'b001010; //slti
26      #20; OPCODE = 6'b001110; //xori
27      #20; OPCODE = 6'b001111; //ori
28      #20; OPCODE = 6'b001100; //andi
29      #20; Fun = 6'b000000; //interval
30      #20; OPCODE = 6'b100011; //lw
31      #20; OPCODE = 6'b101011; //sw
32      #20; OPCODE = 6'b000101; //bne
33      zero = 0; //ne
34      #20; OPCODE = 6'b000101; //bne
35      zero = 1; //eq
36      #20; OPCODE = 6'b000100; //beq
37      zero = 0; //ne
38      #20; OPCODE = 6'b000100; //beq
39      zero = 1; //eq
40      #20; OPCODE = 6'b001000; //addi
41      #20; OPCODE = 6'b010000; //eret
42
43      end

```

## SCPU\_ctrl simulation results

  


 


Simulation results are as expected

## Top

### Top-level structure

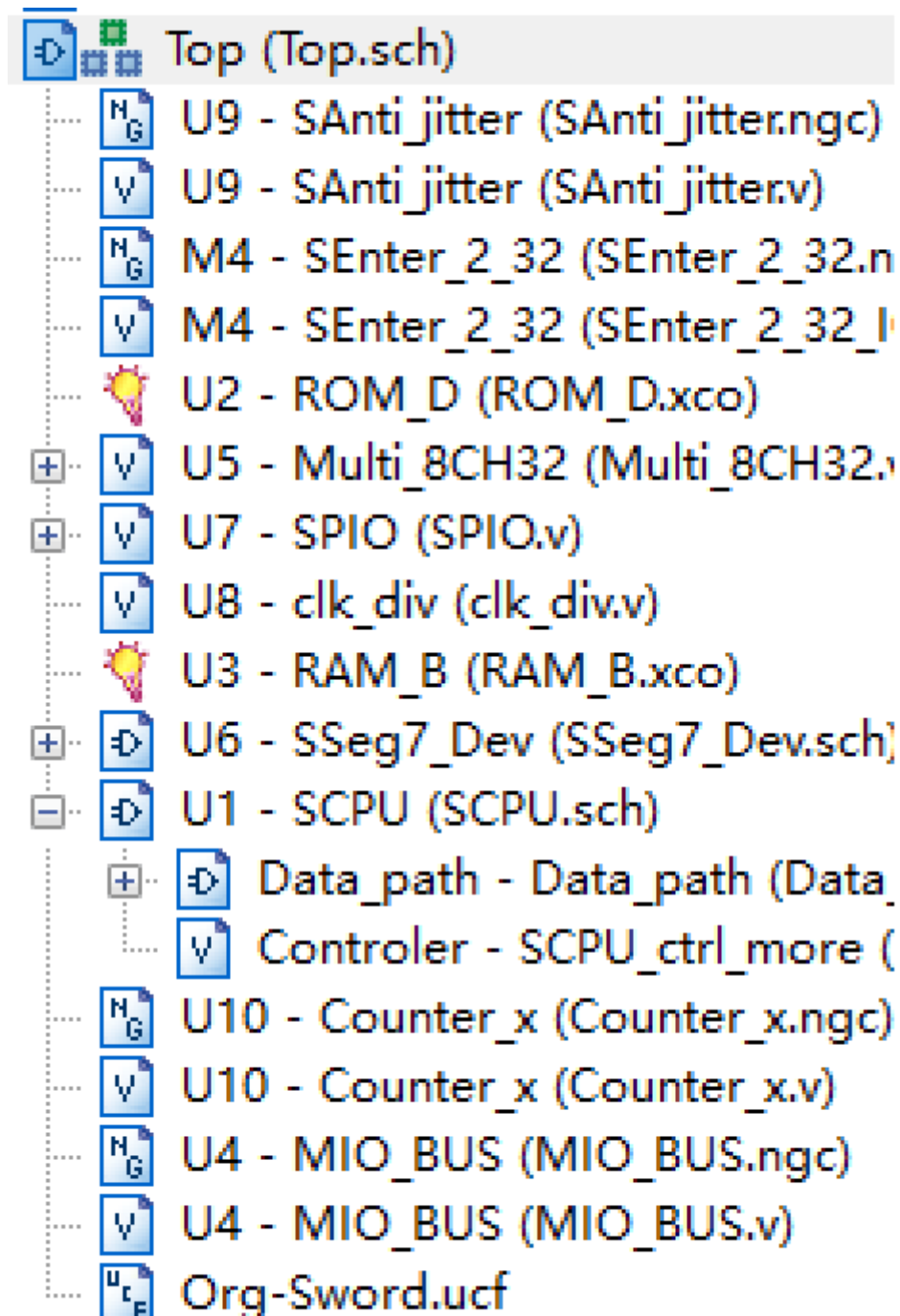

Verified

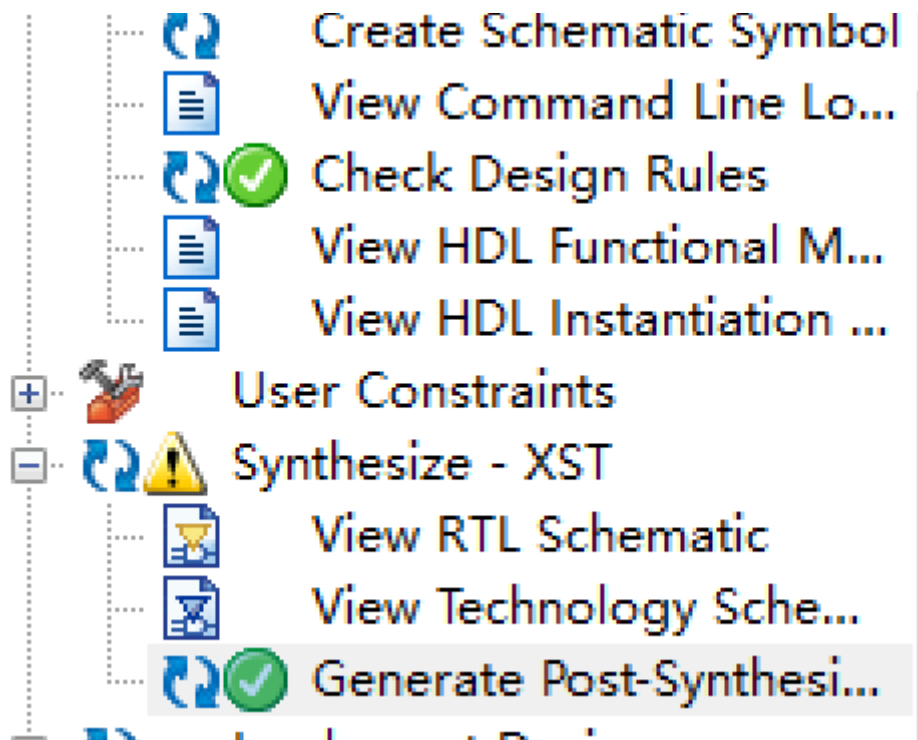

Generate Post-Synthesis Simulation Model successfully

## 四、 讨论与心得

1. Through this experiment, I have a deeper understanding of the design of the logic diagram. For example, you cannot connect the same line at the entrance and exit of a component. 1'b1 can be renamed with the line connected by vcc, 1'b0 can be renamed with the line connected by gnd.
2. In the process of simulation, I have a more in-depth understanding of the implementation of instructions.
3. I learned the verilog grammar of `define, and my skill of cable has also improved.